

# LAB - Manual 18

Required Tools :

Bread board

wires.

Logic gates.

Battery / power.



⇒ A flip flop is an electronic circuit unit with two stable states that can be used to store binary data.

⇒ The stored data can be changed by applying varying inputs.

⇒ Flip flop maintains their ~~state~~ state indefinitely until an input pulse called trigger is received.

⇒ When a trigger is received the flip flop outputs change state according to defined rules and remain in these states until another trigger is received.



## (Types of Flip Flop)

* RS	Flip Flop
* JK	Flip Flop
* D	Flip Flop
* T	Flip Flop

## Clock

⇒ In synchronous device, the exact times at which any output change states are controlled by a signal commonly called clock.

⇒ Clock signals are generally a rectangular pulse train or square wave.

Change state High to low is called negative transition.

## (Triggering Methods)

- \* Level triggering
- \* Edge triggering

### 1 \* level triggering

circuit respond to change in their input (E) held at an active level which may be steady high or low.

SR - flip flop



## Types of level triggering.

+ve level triggering.

⇒ output of a flip flop respond to the input changes only when clock inputs are high (1)

## -ve level triggering.

⇒ output of a flip flop respond to the input changes only when clock inputs are low (0) level.

## ② Edge triggering

⇒ Flip flop which changes its output only corresponding to +ve (rising) or -ve (falling) edge of the clock input.

### Types of Edge triggering

#### -ve edge triggering

⇒ Flip flop which allows its ~~output~~ output to change in response to inputs only at the instants corresponding to rising edge of clock.


(Positive spike) its output will not respond to change in inputs at any other instant of the time.



-ve edge triggering

Flip flop which responds only to the falling edge of clock (negative spikes) of the clock.

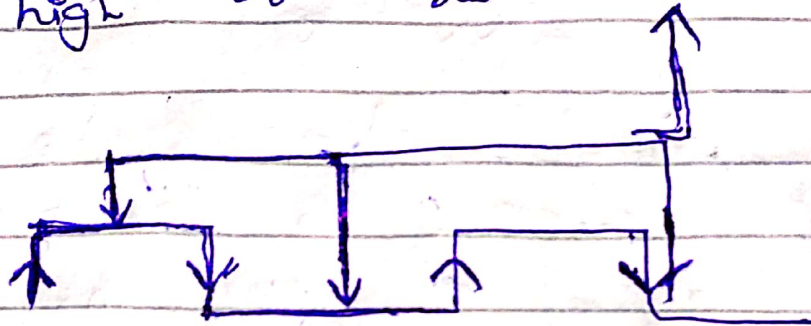output changes when clock input is high or low




=> The edge triggered flip flop sample input at the +ve or -ve edge and changes its output according

(Difference b/w Latches and Flip flop)

\* A latch and a flip flop is  
a gating or clocking mechanism.

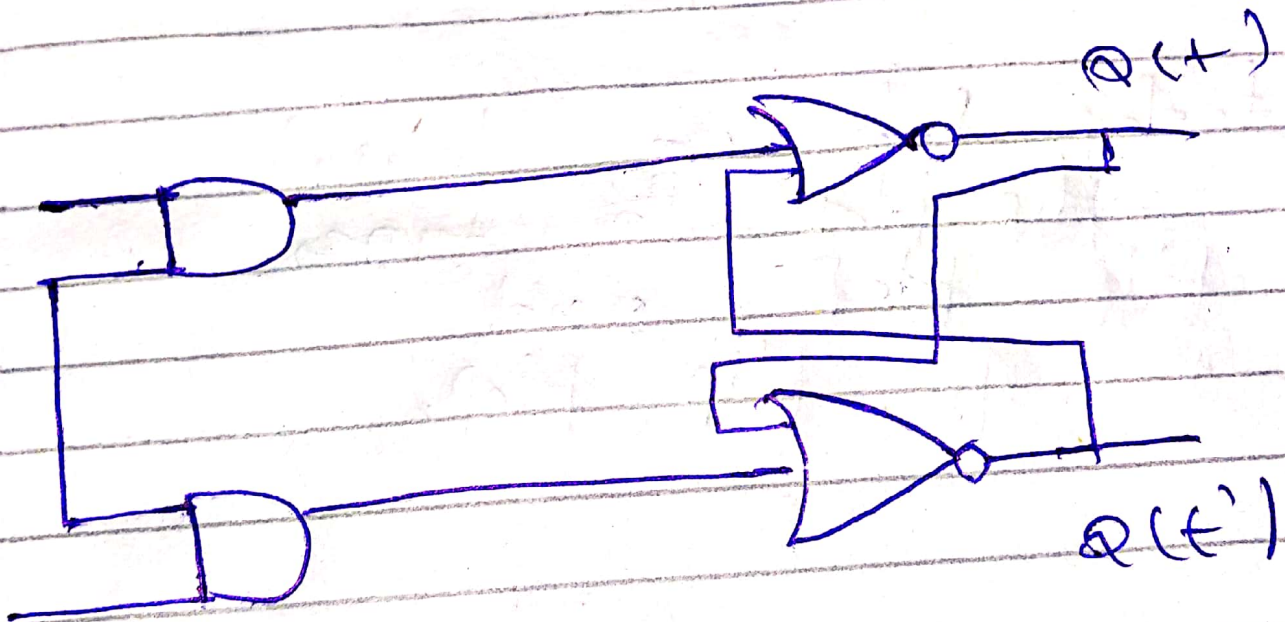\* Latch is level-triggered and  
flip flop is edge triggered





# Applications

- \* counters
- \* frequency dividers.
- \* shift registers.
- \* Storage Registers.
- \* Data storage

## Conclusion

In today lab we learnt about flip flop its type of flip flop and working of flip flop.