

# (Universal GATES)

⇒ There are two universal gates

- (1) NAND (2) NOR

⇒ Universal Means we can make any gate using NAND gate and NOR GATE

⇒ Making All other gates with

(NAND GATE)


$$Y = \overline{A \cdot B}$$




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

① ~~Not~~ NOT GATE with NAND GATE

⇒ we just have to join the inputs

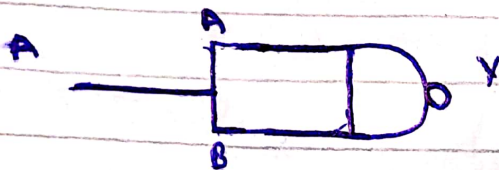


Exp ①

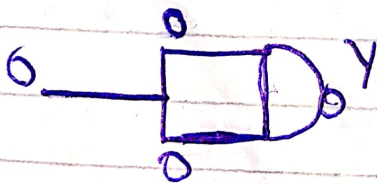

0 0 = 1


Exp ②

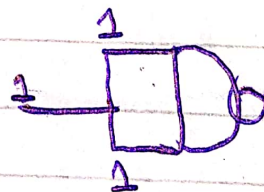

1 1 = 0


⇒ it is behaving like NOT gate

## ② (AND GATE with NAND GATE IC)

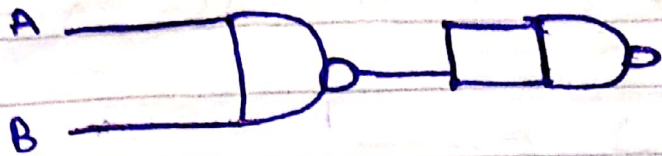

⇒ Two NAND GATE = AND GATE



Exp 1

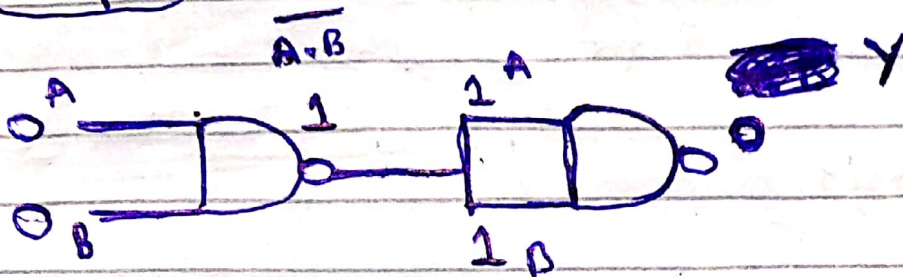

Means

A	B	Y
0	0	0

Exp 2

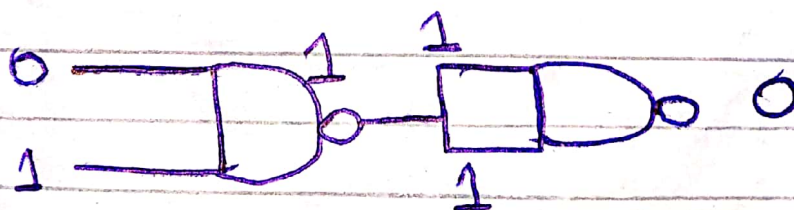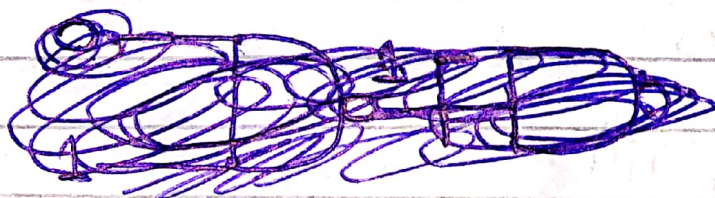

Means


A	B	Y
0	1	0

⇒ it is behaving like AND GATE




### ③ OR GATE using NAND IC

=> 3-NAND = OR-GATE

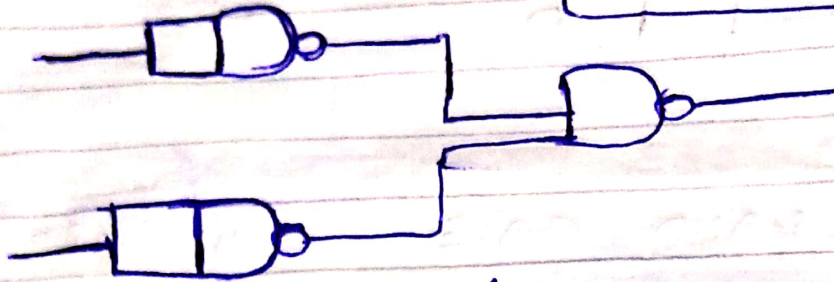

=> Two ~~one-input~~ And gates and  
3rd ~~and~~ and gate

Exp-1

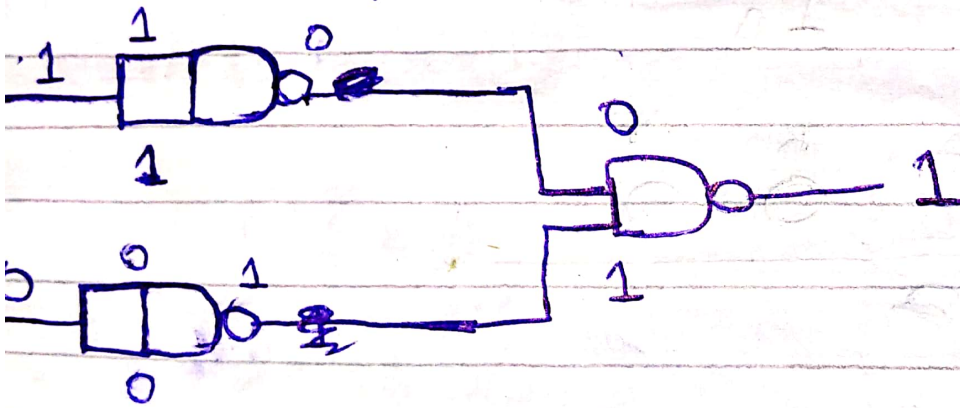


A	B	Y
1	0	1


just like OR gate

# (NOR GATE using NAND-IC)

4-NAND = NOR

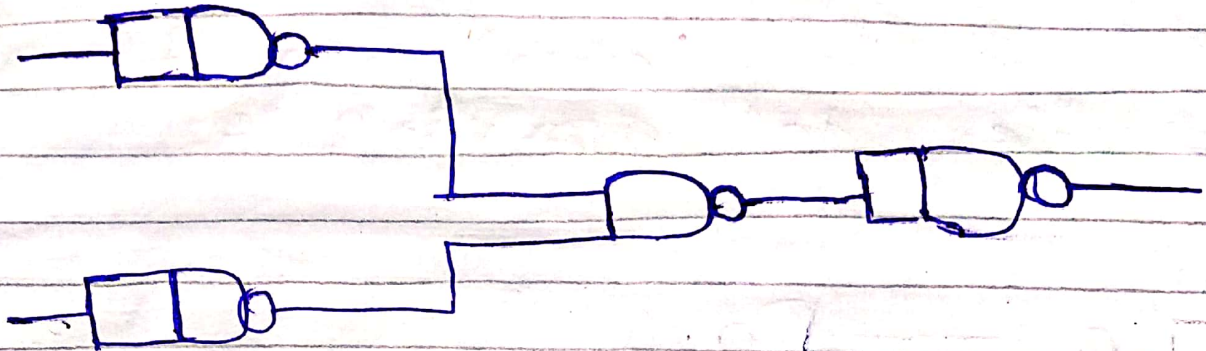

Exp-1

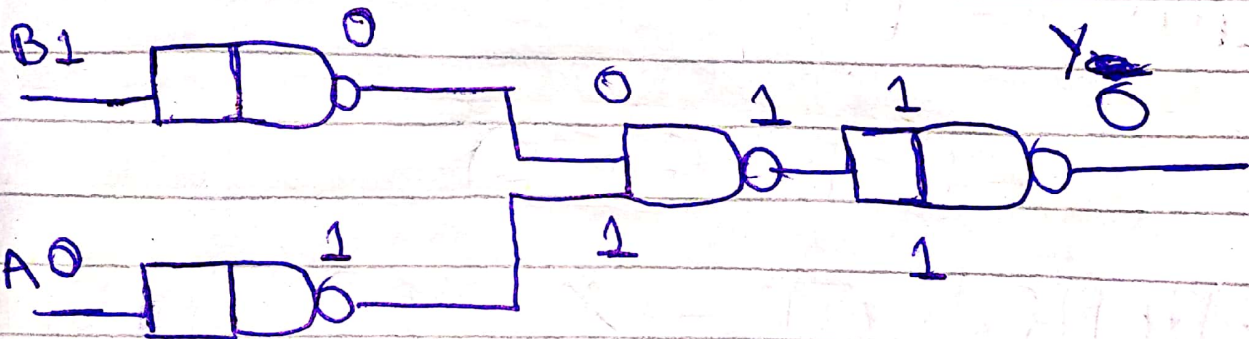



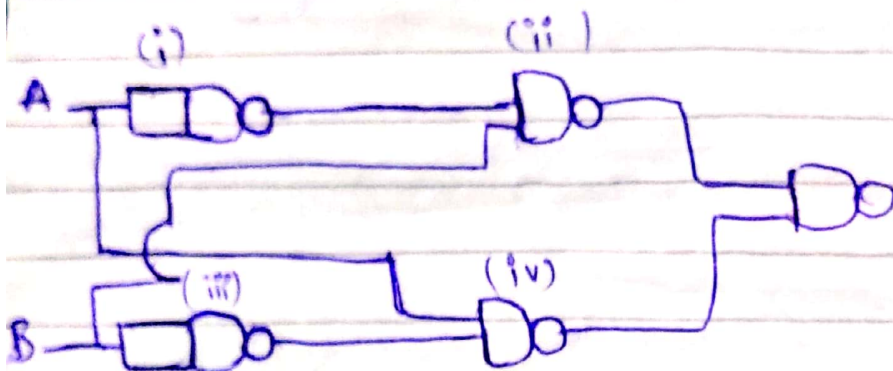
## (EX-OR using NAND-GATE)


$$5\text{-NAND} = \text{X-OR}$$

= just give its connection of ~~2~~ 1-gate to ~~4~~ 4-gate



## (EX-NOR GATE)


$$6\text{-NAND GATE} = \text{X-NOR}$$

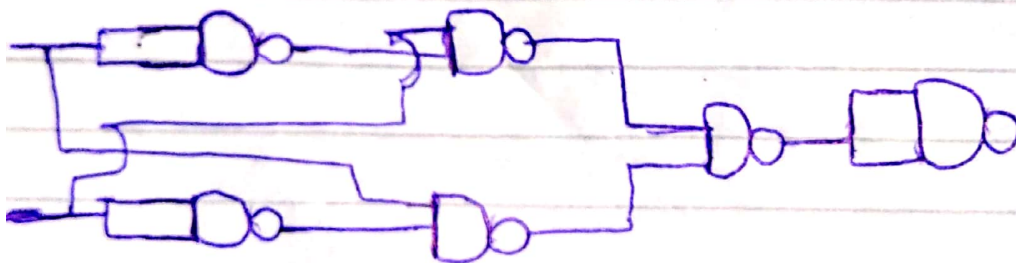

⇒ just add one extra nand gate to the ~~4~~ 5-OR designed circuit.


# (NOR GATE)

(1) NOT GATE using NOR GATE

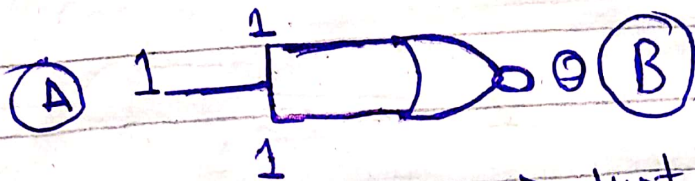


$\Rightarrow$  just short

(2) OR GATE using NOR GATE

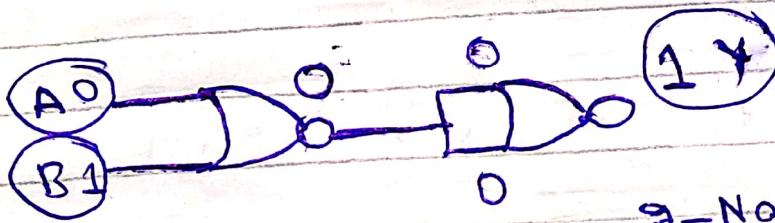


2-NOR = OR

(3) AND GATE with NOR GATE

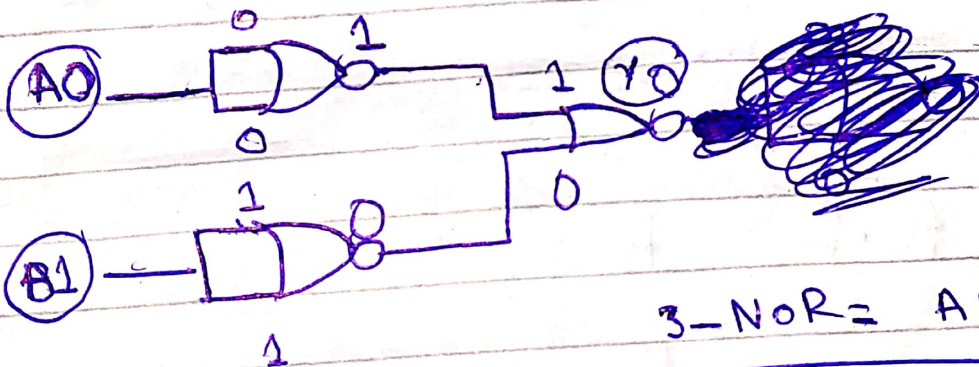


3-NOR = AND

(4) NAND GATE with NOR GATE

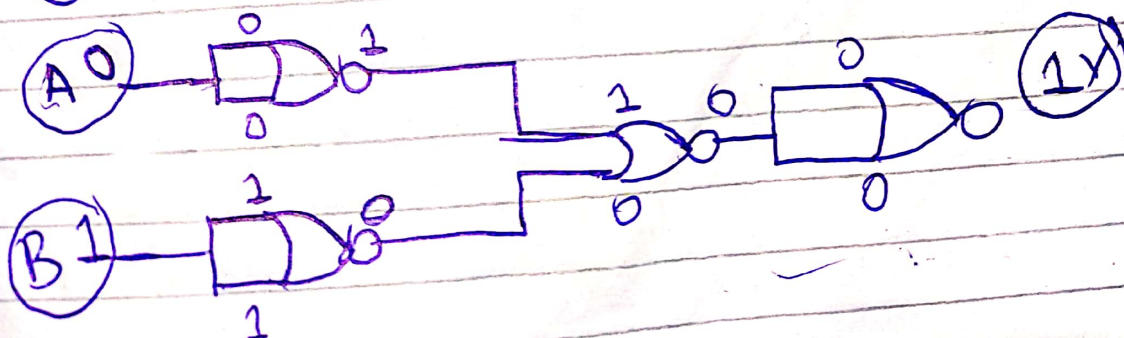



## ⑤ (X-NOR - GATE) - (using NOR GATE)

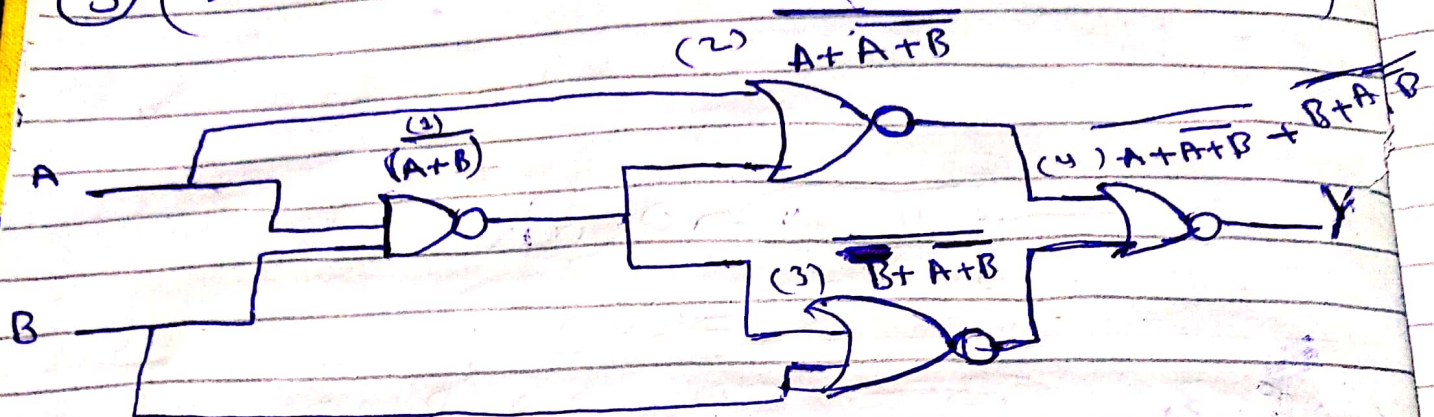

①  $A+B$       ②  $A + A + B$       ③  $B + A + B$

④  $A + A + B + B + A + B$

NOC Demorgan's law is

①  $\overline{A+B} = \bar{A} \cdot \bar{B}$

②  $\overline{A \cdot B} = \bar{A} + \bar{B}$



(Solving eq 4)

$$\Rightarrow A + \overline{A+B} + B + \overline{A+B}$$

using (801)  
De Morgan law

$$\Rightarrow \overline{A} \cdot \overline{A+B} + \overline{B} \cdot \overline{A+B}$$

$$\overline{A} \cdot (A+B) + \overline{B} \cdot (A+B)$$

$$\overline{A} \cdot A + \overline{A} \cdot B + \overline{B} \cdot A + \overline{B} \cdot B$$

Now  $A \cdot \overline{A} = 0$  and  $B \cdot \overline{B} = 0$


$$\Rightarrow \overline{A} \cdot B + \overline{B} \cdot A$$

Now this equation is equal  
to the XOR eq

$$A \oplus B$$



## X-OR GATE using NOR

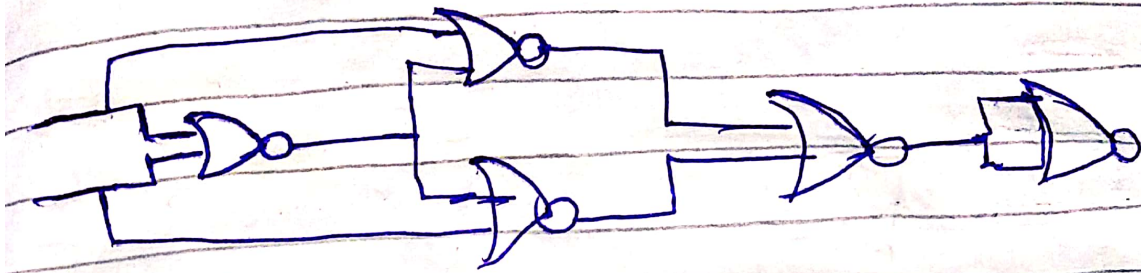

$$\Rightarrow X \text{ NOR } \overline{X} = X \text{ OR } X$$