

LAB - Manual 13

Objective

In this lab we will learn about T-flip flop and registers and their working process and where they work.

⇒ Required Tools.

Logic gates

Wires

Battery / Power

Bread / Board

~~Step~~



⇒ Software

Multisim

T - flip flop

- T - flip flop is the simplified version of JK flip flop. It is obtained by connecting same input "T" to both inputs of JK - flip flop.

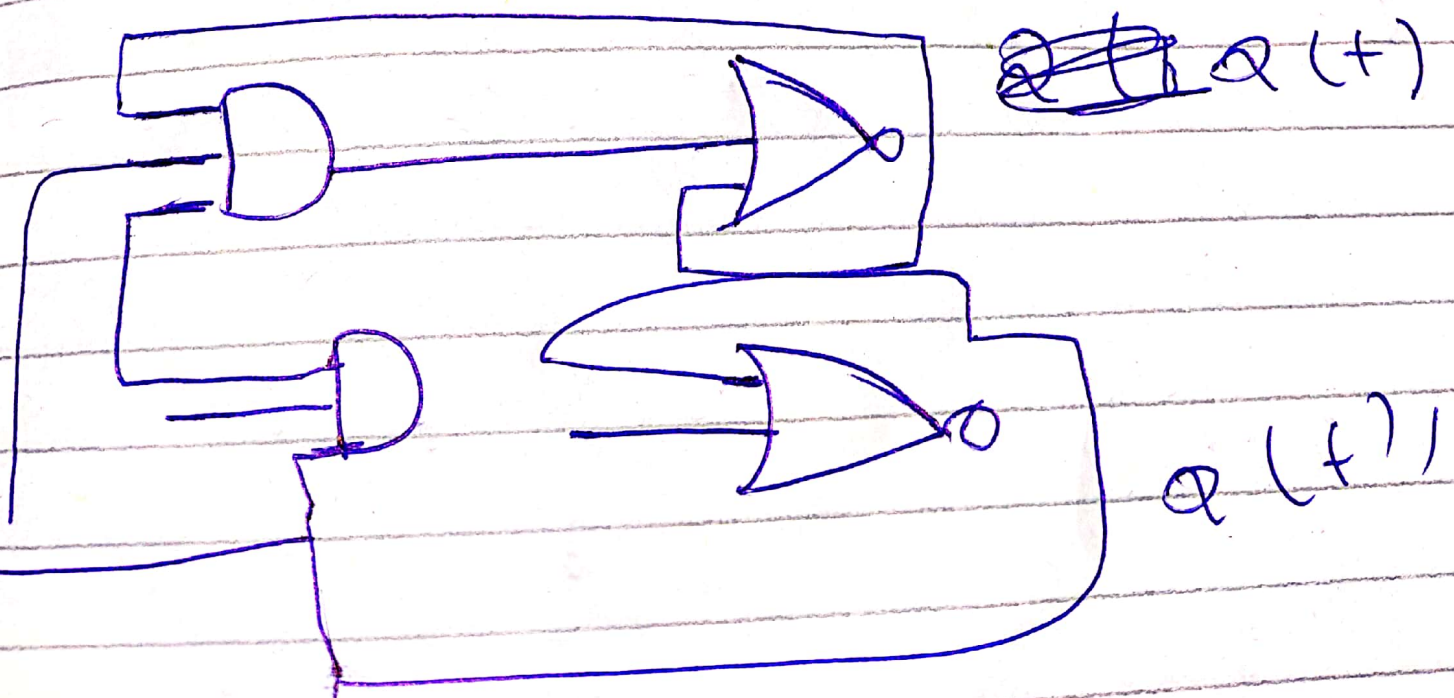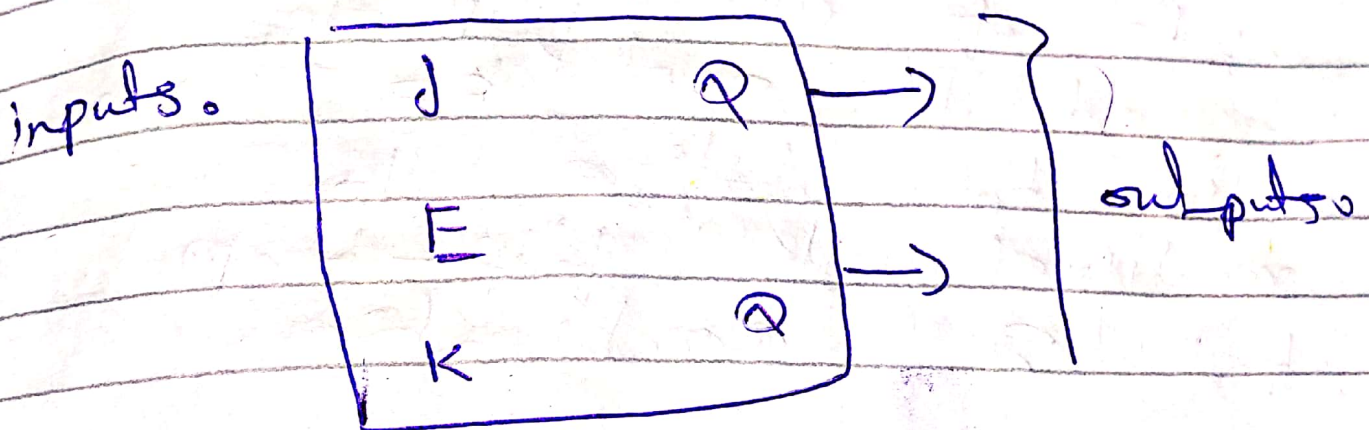- The circuit diagram of T - flip flop is shown in the following figure.



T flip flops.

- This circuit has single input T and two outputs $Q(t)$ and $Q(t')$

The operation of T-flip-flop is same as that of JK-flip flop.

Here we considered the inputs of JK flip flop as $J = T$ and $K = T$ in order to utilize the modified JK flip-flop for a combination

The following table shows the characteristic table of a flip flop

Input	Present state	Next state
0	0	0
0	1	1
1	0	1
1	1	0

From the above characteristics table we can directly write the next state

$$Q(t+1) = T'(Q(t)) + TQ(t)$$

$$= Q(t+1) \oplus Q(t)$$

T- flip flop

The output of T- Flip flop always toggles for every positive transition of the clock signal.

Hence, T flip flop can be used in counters

In this section we implemented various flip flops by providing the cross coupling between NOR gates. Simplifying this you can implement the flip-flop by using NAND gates.

Conclusion

In this lab we learn about T flip flop and working process of T-flip flop and registers.