

# LAB - Manual 9

## Objectives.

=> The objective of this lab is to understand how to make different multiplexers and De-Multiplexer can be obtained and used by using different logic gates.

## Used Equipments.

- \* Wires
- \* Bread Board
- \* Digital experimental board
- \* Logic gates.
- \* Electricity / Battery

## Used Software


- \* ~~Microsoft~~ Mathism
- \* Logicooly.


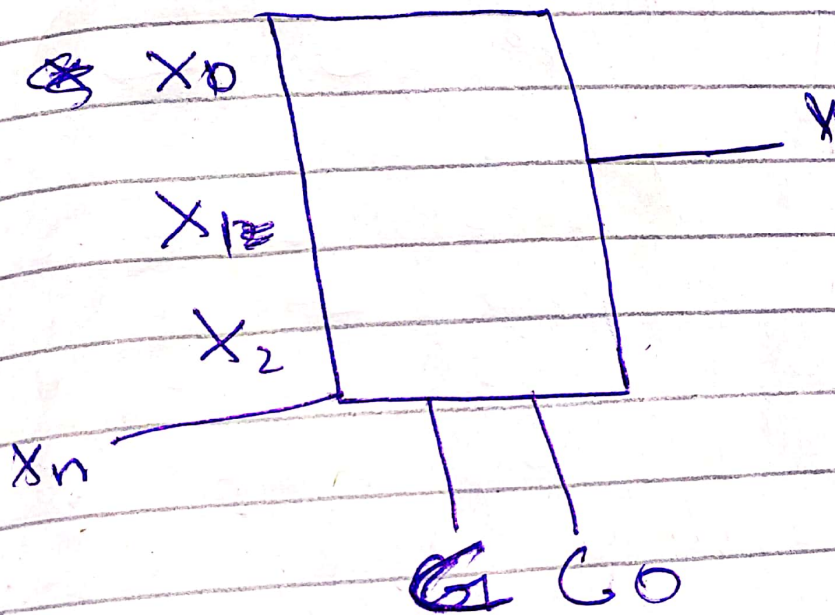
## ( Multiplexer )

⇒ The multiplexer is a device that has multiple inputs and single line output.

⇒ The select lines determines which input is connected to output other words.



### Types


4x1 Mux

8x1 Mux

16x1 Mux
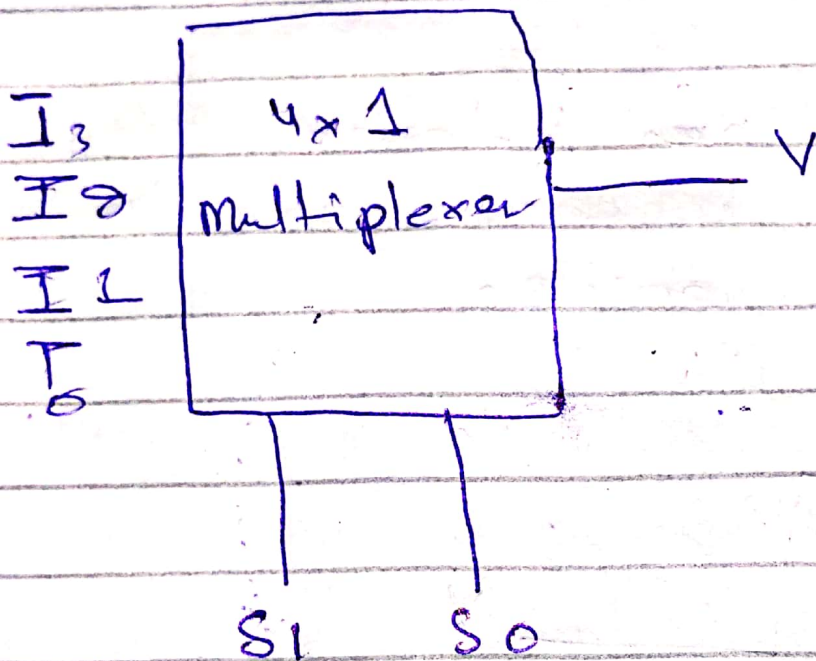
## 4x1 Mux

4x1 mux has four data inputs  $I_3$ ,  $I_2$ ,  $I_1$  and  $I_0$ , Two selection lines  $S_1$  and  $S_0$  and one output  $V$






4x1

Mux

Diagram
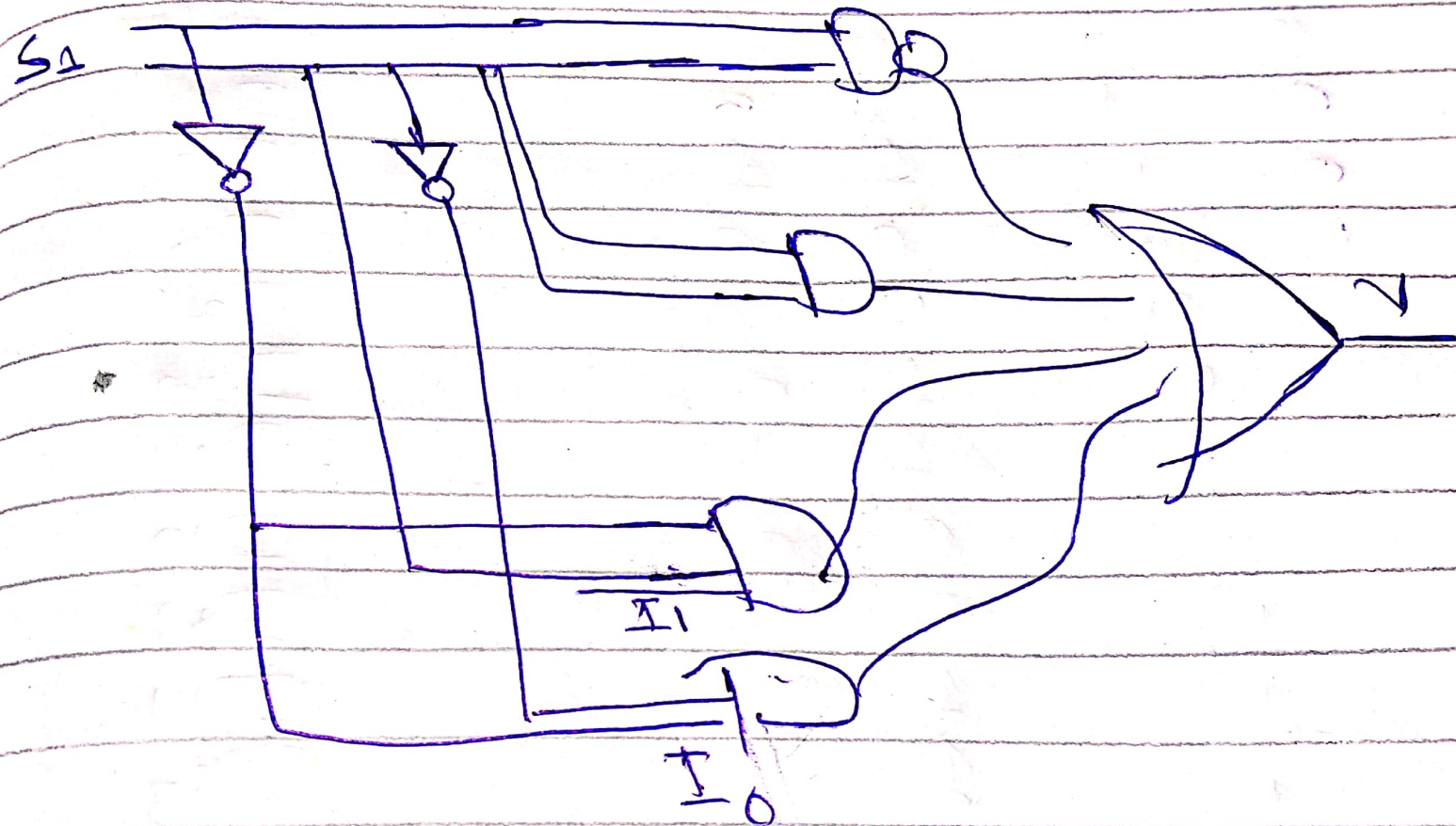
$$Y = S_1' S_0' I_0 + S_1 S_0' I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$



# Mux Truth table

| $S_3$ | $S_2$ | $S_1$ | $S_0$ | $I$      |
|-------|-------|-------|-------|----------|
| 0     | 0     | 0     | 0     | $I_0$    |
| 0     | 0     | 0     | 1     | $I_1$    |
| 0     | 0     | 1     | 0     | $I_2$    |
| 0     | 0     | 1     | 1     | $I_3$    |
| 0     | 1     | 0     | 0     | $I_4$    |
| 0     | 1     | 0     | 1     | $I_5$    |
| 0     | 1     | 1     | 0     | $I_6$    |
| 0     | 1     | 1     | 1     | $I_7$    |
| 1     | 0     | 0     | 0     | $I_8$    |
| 1     | 0     | 0     | 1     | $I_9$    |
| 1     | 0     | 1     | 0     | $I_{10}$ |
| 1     | 0     | 1     | 1     | $I_{11}$ |
| 1     | 1     | 0     | 0     | $I_{12}$ |
| 1     | 1     | 0     | 1     | $I_{13}$ |
| 1     | 1     | 1     | 0     | $I_{14}$ |
| 1     | 1     | 1     | 1     | $I_{15}$ |



# De - Mux

⇒ The function of De-Multiplexer is in contrast to multiplexer function. It takes information from one line and distributes it to a given number of output lines.

It is also called Data Distributor. It has single input  $n$ , select lines, and maximum of  $2^n$  outputs. The input will be connected to one of these outputs based on the selection lines values also known as De-Mux.